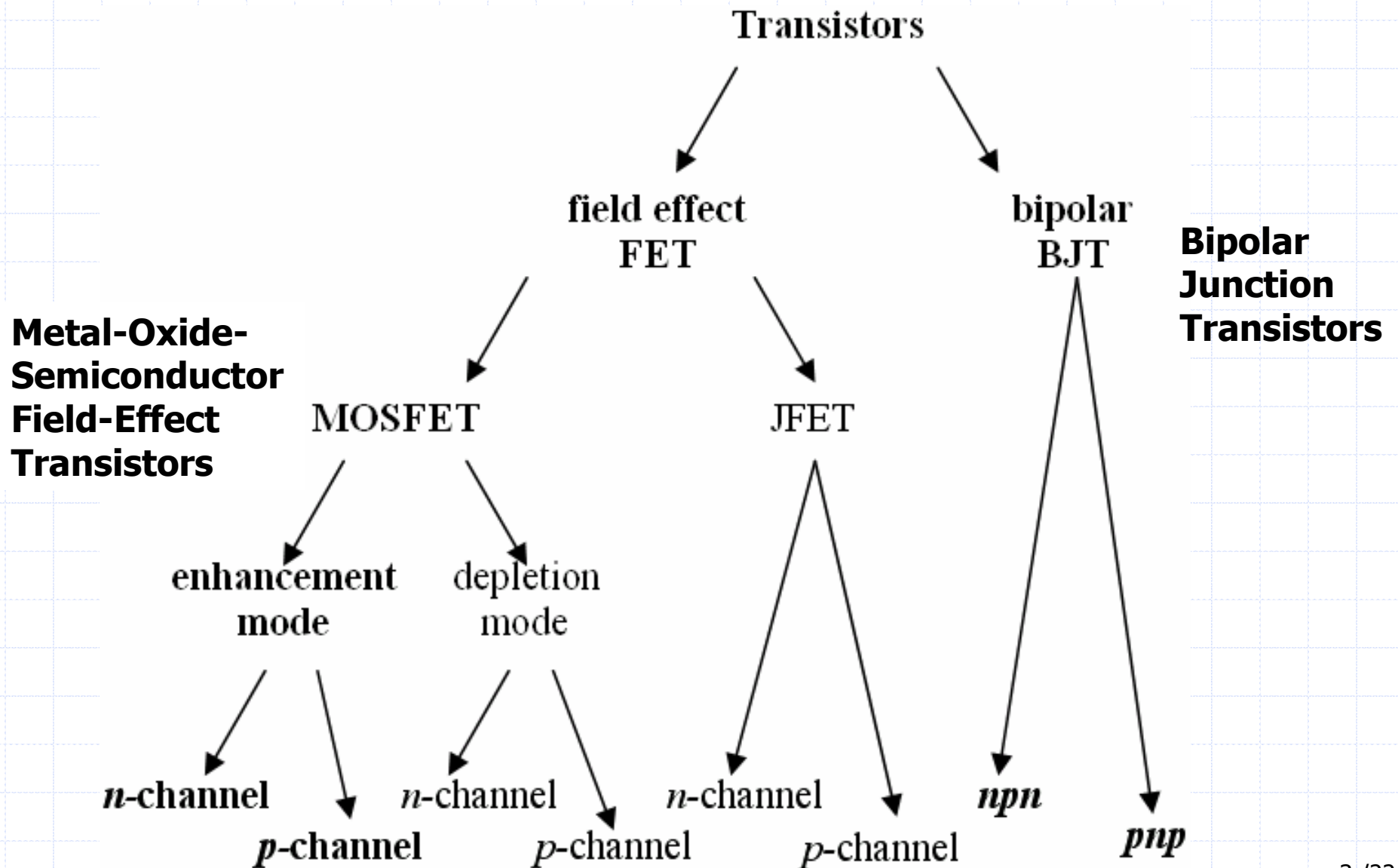


Transistor Digital Circuits

TRANSISTORS

- **active** semiconductor devices (with three terminals)
- Operating **principle**: using a **voltage** between two terminals (command) **to control the current** through the third terminal.
- Transistors: ***voltage-controlled current sources***
- transistors: essential components of every electronic circuit
- Pentium 4 microprocessors : $\sim 43,5$ milion field effect tranzistors
- for the next Intel microprocessors a billion of transistors are anticipated

Transistor types





Operating principle and regions

Transistor – controlled current source

- DC model – ideal voltage controlled current source



n-type

- *n* -channel MOSFET
- *npn* BJT

  

p-type

- *p* -channel MOSFET
- *pn*p BJT

  

Non-linear
controlled sources:
square - MOSFET
exponential – BJT


Using T_n transistor

Why is R necessary ?

Output quantities: I_O V_O

transfer characteristics:

$I_O(V_{CT})$, $V_O(V_{CT})$

 

Transfer Characteristics




- $V_{CT} < V_{Thn}$, T_n - off, $I_O = I_T = 0$
- $V_{CT} > V_{Thn}$, T_n - on, $I_O = I_T > 0$


$$V_{PS} = RI_O + V_O; \quad V_O = V_{PS} - RI_O$$

$$V_{CT} \uparrow, \quad I_O \uparrow, \quad V_O \downarrow$$

$$V_{O,min} = 0$$

$$I_{Oex} = \frac{V_{PS}}{R}$$

   

 

- Two **extreme regions**, passive regions:
 - **cutoff (off)** $I_T=0$; $V_O>0$; ideal switch in off state
 - **extreme conduction (exc)** $I_T=I_{Oex}$; $V_O=0$; ideal switch in the on state


If $V_{CT} < V_{Thn}$ or $V_{CT} > V_{CTex}$ **switching transistor**

- An **intermediary region**, active forward region **a_F**

$V_{CT} \in (V_{Thn}, V_{CTex})$, - **permanent conduction (amplifier)**


Symbols of the transistors

n-type

 


n-channel enhancement-type MOSFET

p-type

 


p-channel enhancement-type MOSFET

G - gate or grid
D - drain
S - source

 



*n*pn BJT

 

*p*np BJT

B – base
C – collector
E – emitter

  The Controlled Switch Model for Transistors



$$v_{CT} > V_{Thn} ; T- (exc) ; i_{OT} > 0 ; v_{OT} \approx 0$$

$$v_{CT} > V_{Thp} ; T- (off) ; i_{OT} = 0$$

$$v_{CT} < V_{Thn} ; T- (off) ; i_{OT} = 0$$


$$v_{CT} < V_{Thp} ; T- (exc) ; i_{OT} > 0 ; v_{OT} \approx 0$$

The controlled switches are **complementary**.


MOSFET DIGITAL CIRCUITS

- Ideal controlled switch model
- Implementation with MOSFET

Logic inverter


 


A	T_n	Y
0	(off)	1
1	(on)	0

 

A	T_p	Y
0	(on)	1
1	(off)	0

  Critical analysis of the inverter with a T_n controlled switch and R



Diminishing the disadvantage:


R as small as possible, ideal $R \rightarrow 0$; R as large as possible, ideal $R \rightarrow \infty$

Solution: replacement of R with a controlled switch


Two solutions:

complementary
switches

complementary
control

 

CMOS

 


TTL


A	T_1	T_2	Y
0	(off)	(on)	1
1	(on)	(off)	0

good bye!
output voltage division
power dissipation

Logic function NAND, NOR

 

 How can we eliminate the disadvantages due to the presence of R ?




CMOS Logic Gates

- CMOS inverter


$$v_{GSn} = v_I$$

$$v_{GSp} = v_I - V_{DD}$$

 


v_I	v_{GSn}	v_{GSp}	T_n	T_p	v_O
0V	$0V < V_{Thn}$	$-V_{DD} < V_{Thp}$	(off)	(on)	$\approx V_{DD}$
V_{DD}	$V_{DD} > V_{Thn}$	$0 > V_{Thp}$	(on)	(off)	$\approx 0V$

NAND

 


A	B	T_{n1}	T_{n2}	T_{p1}	T_{p2}	$Y = \overline{A \cdot B}$
0	0	(off)	(off)	(on)	(on)	1
0	1	(off)	(on)	(on)	(off)	1
1	0	(on)	(off)	(off)	(on)	1
1	1	(on)	(on)	(off)	(off)	0

NOR

 


AND

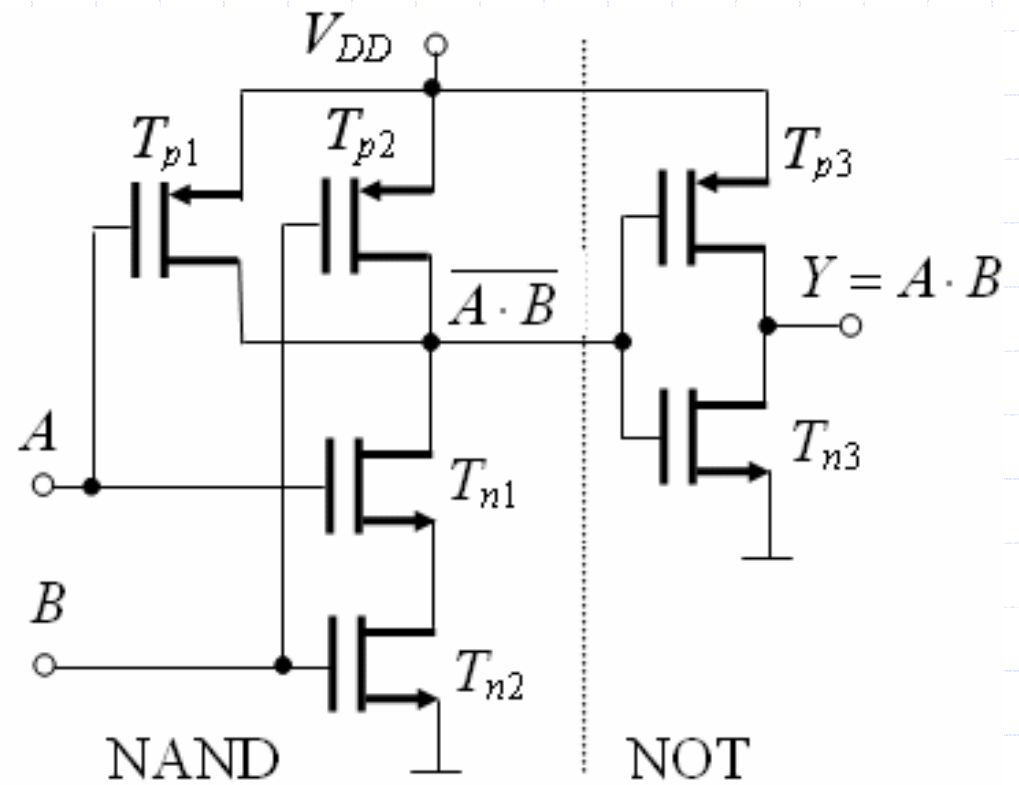

Bipolar Digital Circuits


- Inverter**

 

RTL Technology

v_I	T_n	v_O
0V	(off)	V_{CC}
V_{CC}	(on)	0.2V


- NOR**

 

A	B	T_1	T_2	$Y = \overline{A + B}$
0	0	(off)	(off)	1
0	1	(off)	(on)	0
1	0	(on)	(off)	0
1	1	(on)	(on)	0



TTL: Transistor-Transistor Logic

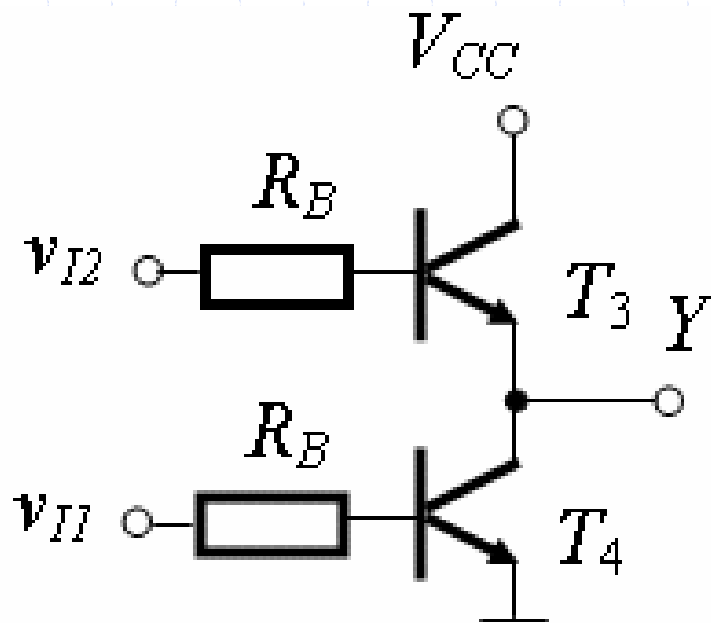- Logic Inverter
 - from technological reasons in TTL integrated circuits the use of only npn type transistors is preferred
 - identical transistors but complementary control




T_3	T_4	Y
(on)	(off)	1
(off)	(on)	0

Standard TTL gate

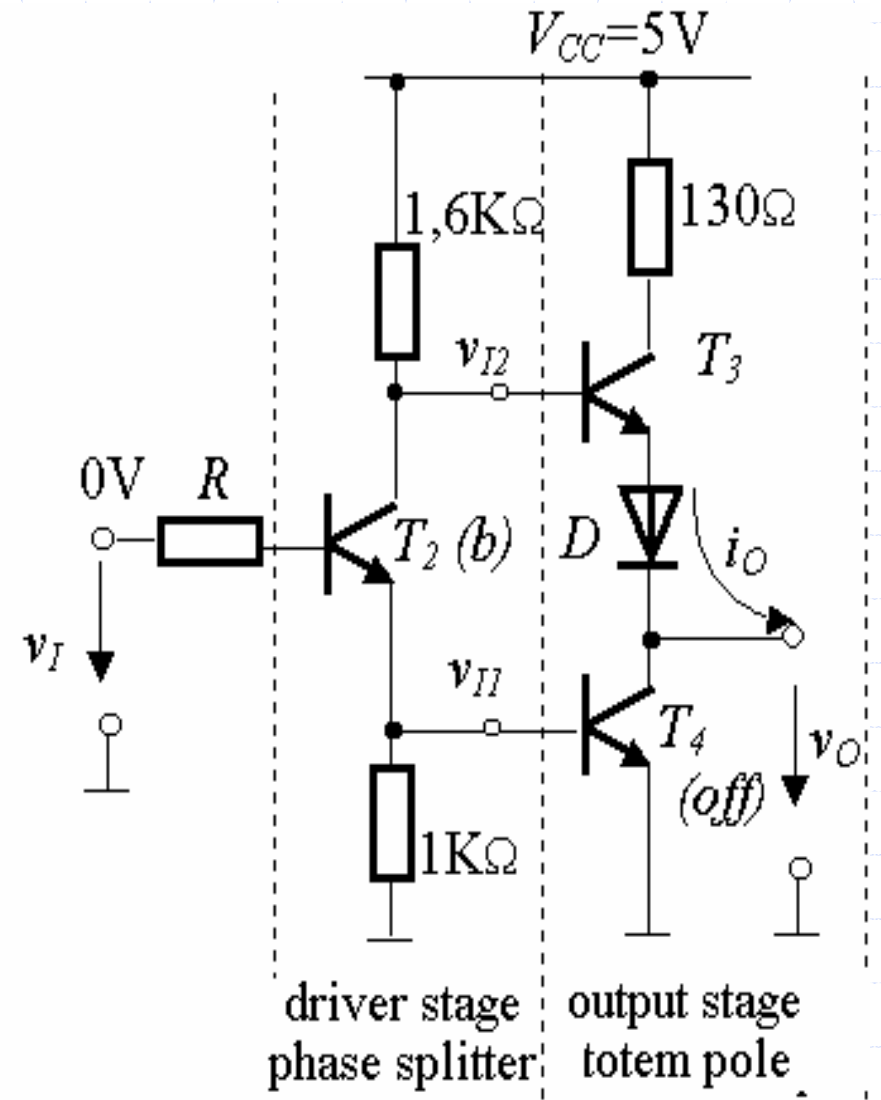 

Noise margins

 

$$NM_H = V_{OHmin} - V_{IHmin}$$

$$NM_L = V_{ILmax} - V_{OLmax}$$

Voltage levels and noise margins for CMOS family operated with 5V

$$NM_L = 1.5V - 0.5V = 1V$$

$$NM_H = 4.5V - 3.5V = 1V$$

The voltage levels and noise margins for TTL family

